

CS100 #04


# Logic Gates

Vadim Surov

# Introduction


- We have looked at Boolean expressions in abstract terms.
- In this presentation, we see that Boolean functions are implemented in digital computer circuits called gates.
- A gate is an electronic device that produces a result based on two or more input values.
  - In reality, gates consist of one to six transistors, but digital designers think of them as a single unit.
  - Integrated circuits contain collections of gates suited to a particular purpose.

# Logic Gates AND

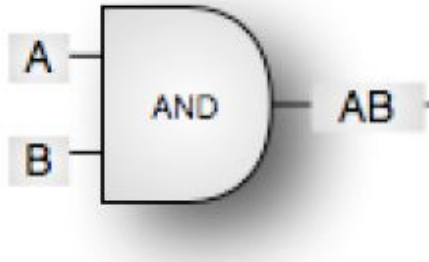


A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

# Logic Gate OR

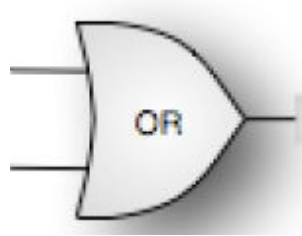

A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1


# Logic Gate NOT

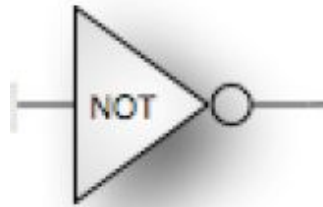


A	NOT A
0	1
1	0
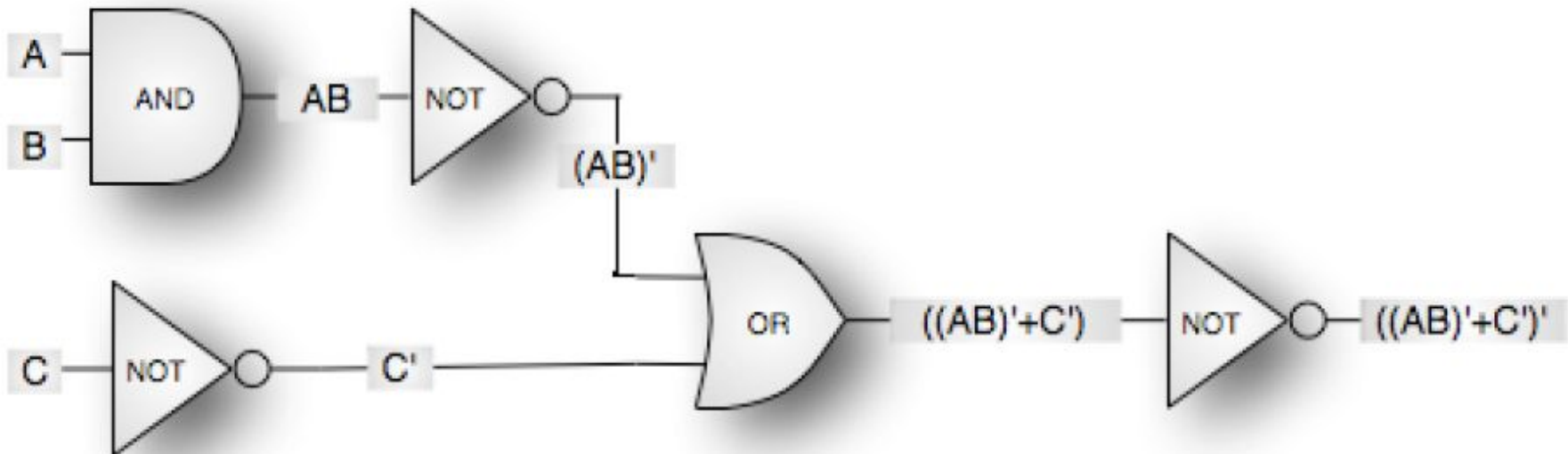
# Combinational Circuits

- The main thing to remember is that combinations of gates implement Boolean functions.
- The circuit below implements the Boolean expression




# Combinational Circuits

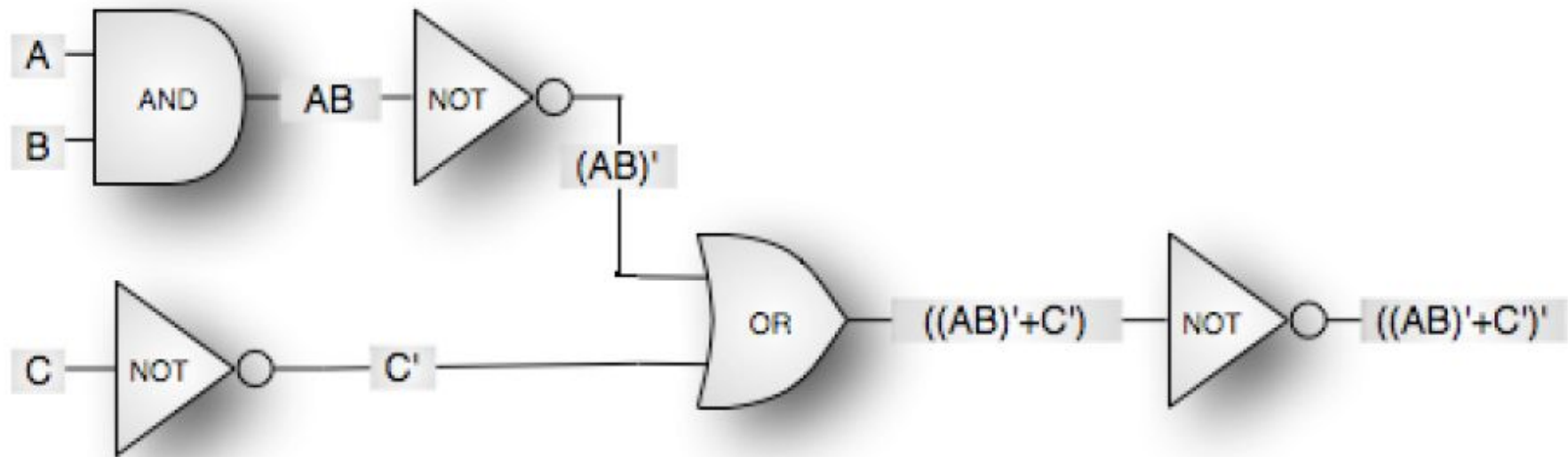

A	B	C	AB	C'	AB'	$((AB)' + c')$	$((AB)' + c')'$
0	0	0	0	1	1	1	0
0	0	1	0	0	1	1	0
0	1	0	0	1	1	1	0
0	1	1	0	0	1	1	0
1	0	0	0	1	1	1	0
1	0	1	0	0	1	1	0
1	1	0	1	1	0	1	0
1	1	1	1	0	0	0	1
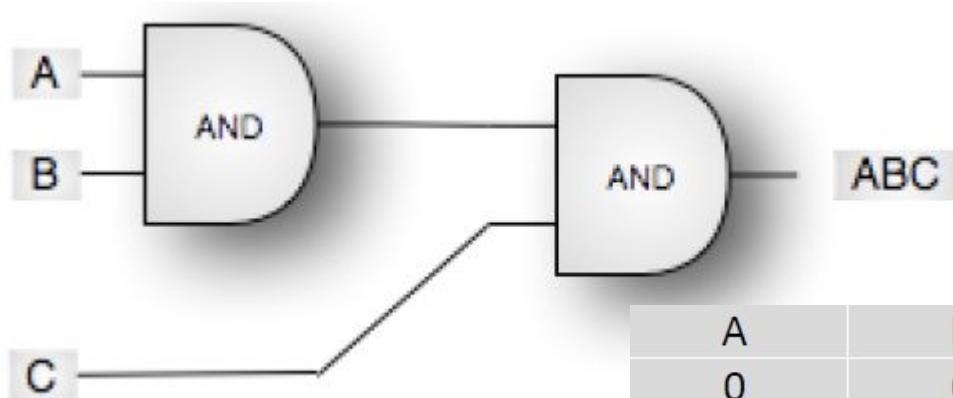
# Combinational Circuits

- Compare previous circuit to the following one, you will find that they are equivalent, they produce similar outputs:



A	B	C	AB	ABC
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	1



# Combining Logical Gate: NAND

$$(A \cdot B)'$$



A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

# Combining Logical Gate: NOR

$$(A + B)'$$




A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

# Combining Logical Gate: XOR

$$A \cdot B' + A' \cdot B$$

$$(A + B) \cdot (A' + B')$$


$$(A + B) \cdot (A \cdot B)'$$

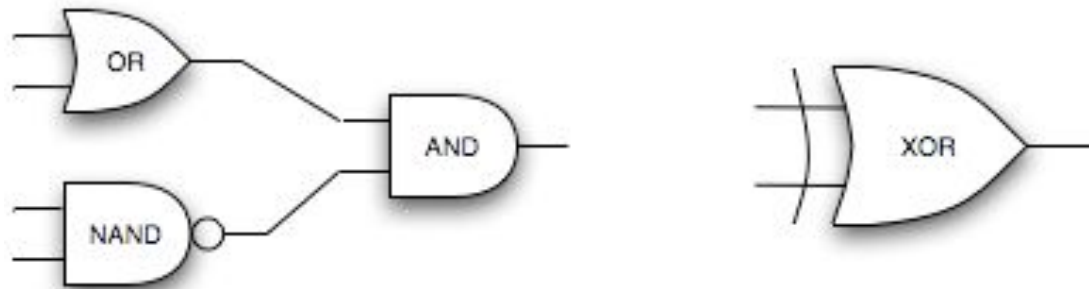

0	0	0
0	1	1
1	0	1
1	1	0

# Combining Logical Gate: XNOR

$$(A + B)' + (A \cdot B)$$

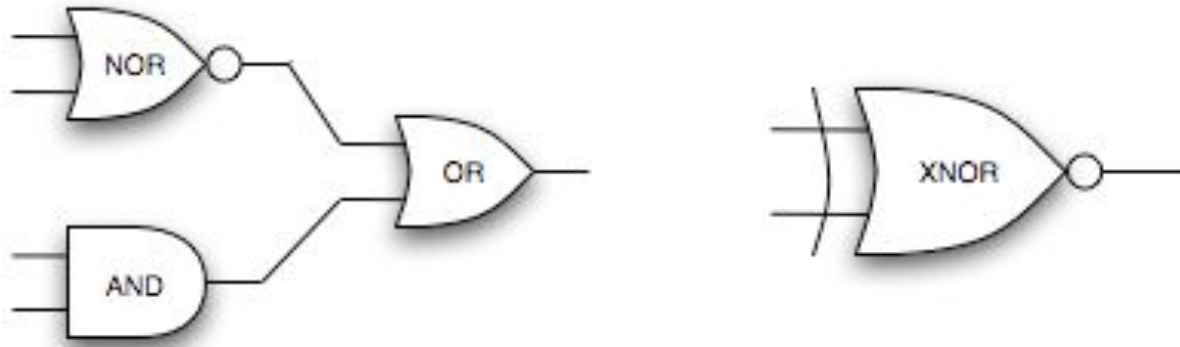

<i><b>A</b></i>	<i><b>B</b></i>	<i><b>XNOR</b></i>
0	0	1
0	1	0
1	0	0
1	1	1